

# EE210: Analog Electronics - Quiz 3

NAME (in capital)

Roll No

Time: 15 minutes

1) : Consider the circuit in Fig. 1. A three terminal non-linear element has been used, whose terminals are defined in the inset. The element has the following characteristics.

$$I_D = I_S = \alpha V_{GS}^2 \text{ for } V_{GS} \geq 0 \text{ and } V_{DS} \geq 0. \quad I_D = I_S = 0 \text{ otherwise.}$$

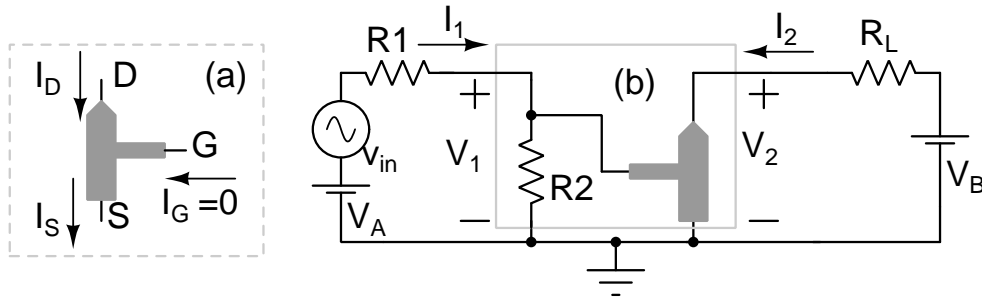


Fig. 1. Problem 1

a) : Assume  $V_A = 2V$ ,  $V_B = 5V$ ,  $R_1 = R_2 = 1k\Omega$ ,  $\alpha = 2mA/V^2$  and  $R_L = 1k\Omega$ . Find the small-signal two-port y-parameters of the network within the box (in Fig. 1(b)) and sketch the small-signal two-port network. [6]

Same as set in approach

$$y_{11} = 1mS$$

$$y_{12} = 0$$

$$y_{21} = 4mS$$

$$y_{22} = 0$$

..contd..

b) : If  $v_{in} = 10mV \sin(\omega t)$ , find the small signal voltage across  $V_1$  and  $V_2$ .

[4]

Approach same as set 1

$$V_1 = 5mV \sin(\omega t)$$

$$V_2 = -20mV \sin(\omega t)$$