

EE210: Analog Electronics - Quiz 3

NAME (in capital)

Roll No

Time: 15 minutes

1) : Consider the circuit in Fig. 1. $V_{DC} = 5V$. A three terminal non-linear element has been used, whose terminals are defined in the inset. The element has the following characteristics.

$$I_D = I_S = \alpha V_{GS}^2 \text{ for } V_{GS} \geq 0 \text{ and } V_{DS} \geq 0. \quad I_D = I_S = 0 \text{ otherwise.}$$

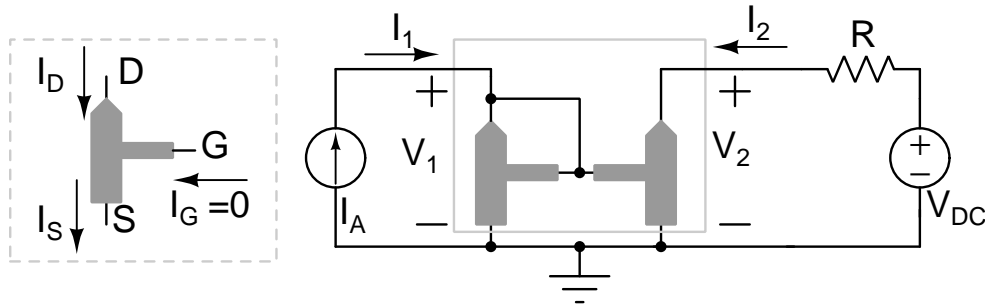


Fig. 1. Problem 1

a) : Assume $I_A = 2mA$, $\alpha = 2mA/V^2$ and $R = 0.5k\Omega$. Find the small-signal two-port y-parameters of the network within the box (in Fig. 1(b)) and sketch the small-signal two-port network. [6]

Approach is same as Set 1.

$$y_{11} = 4mS$$

$$y_{12} = 0$$

$$y_{21} = 4mS$$

$$y_{22} = 0$$

..contd..

b) : If $I_A = 1 \text{ mA} + 0.1 \text{ mA} \sin(\omega t)$, find the small signal voltage across V_1 and V_2 . [4]

Approach same as set-1

$$V_1 = \frac{i_{in}}{y_1} = 250 \text{ mV} \sin(\omega t)$$

$$V_2 = -y_{21} V_1 R = -0.05 \text{ V} \sin(\omega t)$$