

# EE210A: Microelectronics I - Mini-Quiz 4

NAME (in capital)

Roll No

Time: 20 minutes

1) : For the transistor in the following circuit  $\mu_n C_{ox} = 200 \mu A/V^2$ ,  $V_{tn} = 1V$ , Also,  $V_{DD} = 5V$ .

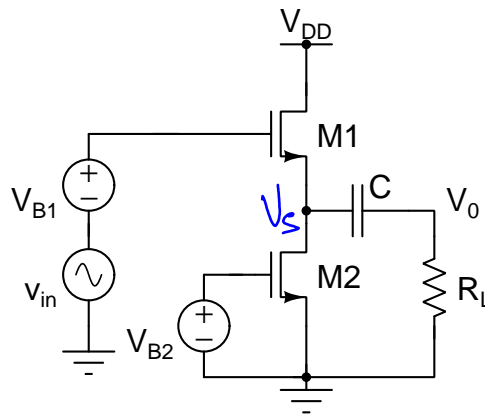


Fig. 1. Problem 1

a) : Assume  $W/L = 10$  for both transistors. Find the minimum  $V_{B1}$  and  $V_{B2}$  such that a quiescent current of 1 mA flows through stack while keeping both transistors in saturation. [3]

$$\text{For } M2 \Rightarrow V_{B2} = V_{tn} + \sqrt{\frac{2 I_D}{\mu_n C_{ox} (W/L)_2}}$$

$$= 1 + \sqrt{\frac{2 \times 1m}{0.2 \times 10}} = 2V$$

For minimum  $V_{B1}$ ,  $V_s$  has to be minimum.

$$\therefore V_{B1} - V_s = V_{tn} + \sqrt{\frac{2 I_D}{\mu_n C_{ox} (W/L)_1}}$$

$$\Rightarrow V_{B1}(\min) = V_{smin} + 2V$$


$$V_{smin} = V_{B2} - V_{tn} = 1V \quad \therefore V_{B1}(\min) = 3V.$$

b) : What changes in the  $W/L$  would you do to ensure M2 is away from the edge of saturation region by 500 mV while maintaining 1 mA of quiescent current? [4]

Must increase  $V_S \Rightarrow$  Must reduce  $V_{ov}/m_1$   
 (∵  $V_{B1}$  is constant)

$$\begin{aligned} \therefore V_S &= V_{B1} - (V_{th} + V_{ov1}) \\ \Rightarrow 1.5 &= 3 - \left(1 + \sqrt{\frac{2 I_{D1}}{\mu C_{ox} (W/L)_1}}\right) \\ \Rightarrow \sqrt{\frac{2 \times 1 \text{ mA}}{0.2 \text{ m} + (W/L)_1}} &= 0.5 \\ \Rightarrow (W/L)_1 &= 40 \end{aligned}$$

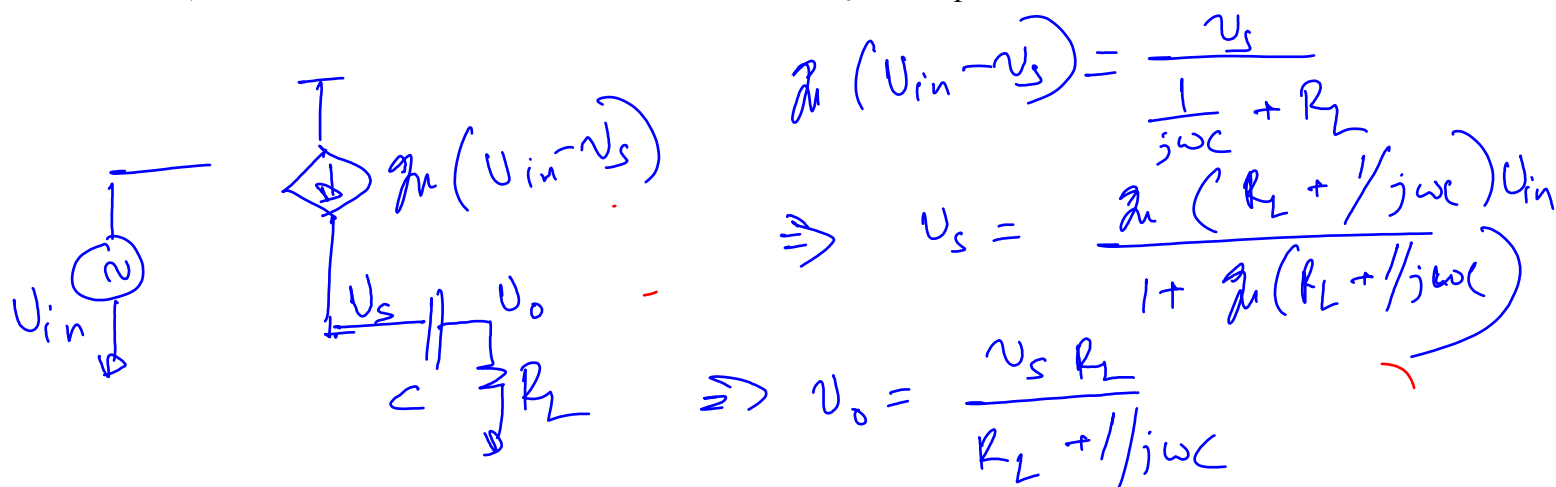c) : What is the constraint on  $R_L$  to ensure that  $v_o$  is independent of  $R_L$ ? [3]



$$\begin{aligned} g_m (U_{in} - V_S) &= \frac{V_S}{\frac{1}{j\omega C} + R_L} \\ \Rightarrow V_S &= \frac{g_m (R_L + 1/j\omega C) U_{in}}{1 + g_m (R_L + 1/j\omega C)} \end{aligned}$$

$$\Rightarrow v_o = \frac{V_S R_L}{R_L + 1/j\omega C}$$

$$\therefore R_L \gg 1/\omega C$$

$$\text{and } g_m R_L \gg 1$$

$$\Rightarrow R_L \gg 1/g_m$$

It's okay if someone has assumed  $C \rightarrow \infty$  and done the analysis.

$$= \frac{U_{in} g_m R_L}{1 + g_m (R_L + 1/j\omega C)}$$