

EE210: Analog Electronics - Quiz 7

NAME (in capital)

Roll No

Time: 15 minutes

1) : All transistors in the figures are biased in saturation (biasing network has not been shown). Assume transconductance of $M1$ is g_{m1} and that of $M2$ is g_{m2} . Neglect CLM.


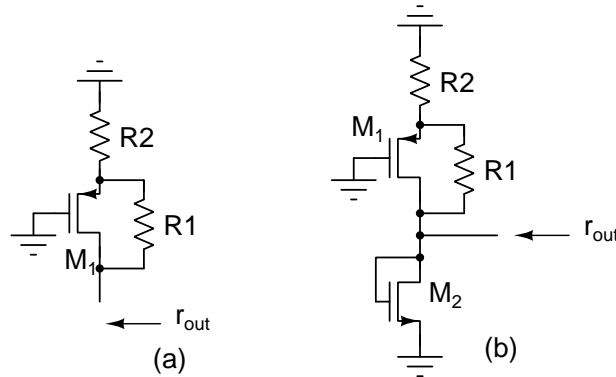


Fig. 1. Problem 1

a) : Find the small-signal output resistance as indicated in Fig. (a).

[6]

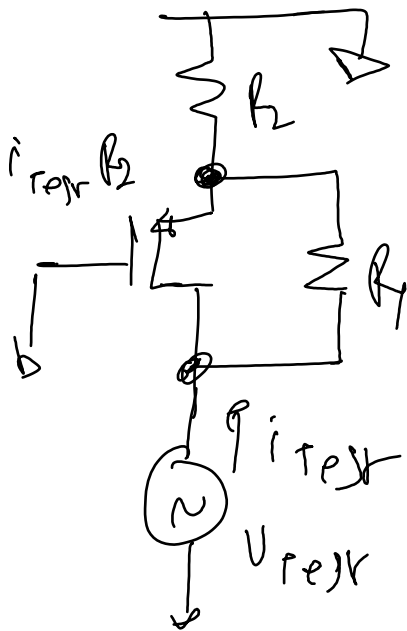

KCL @ V_{test}

$$i_{test} = \frac{V_{test} - i_{test} R_2}{R_1} + g_{m1} R_1 (0 - i_{test} R_2)$$

$$\Rightarrow \frac{V_{test}}{i_{test}} = R_1 + R_2 + (g_{m1} R_1) R_2$$

$$= R_{out1}$$

contd..

b) : Find the small-signal output resistance as indicated in Fig. (b).

[4]

