

# EE210A: Microelectronics I - Mini-Quiz 5

NAME (in capital)

Roll No

Time: 15 minutes

1) : Consider  $\mu_n C_{ox} = 200 \mu A/V^2$ ,  $I_0 = 1mA$ ,  $V_{tn} = 1V$ ,  $V_B = 2.5V$ .

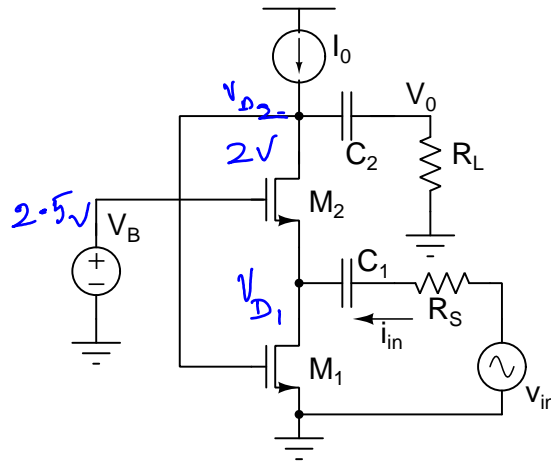


Fig. 1. Problem 1

a) : Size  $M1$  and  $M2$  such that under quiescent conditions  $M1$  is in saturation with a margin of 200 mV, and  $M2$  is in saturation with margins of 500 mV. [4]

$$\text{For } M2, \quad V_{D2} = V_B - V_{tn} + 500mV = 2V$$

$$\text{For } M1 \quad V_{D2} = V_{tn} + \sqrt{\frac{2I_0}{\mu_n C_{ox} (W/L)_1}}$$

$$\Rightarrow 2 = 1 + \sqrt{\frac{2 \times 1m}{0.2m (W/L)_1}}$$

$$\Rightarrow (W/L)_1 = 10$$


$$V_{D1} = V_{D2} - V_{tn} + 200mV = 1.2V$$

$$\text{For } M2 : \quad V_{D2} = V_{tn} + \sqrt{\frac{2I_0}{\mu_n C_{ox} (W/L)_2}}$$

$$\Rightarrow V_B - V_{D1} = V_{tn} + \sqrt{\frac{10}{(W/L)_2}}$$

$$\Rightarrow 2.5 - 1.2 - 1 = \sqrt{\frac{10}{(W/L)_2}} \Rightarrow (W/L)_2 = \frac{10}{0.09}$$

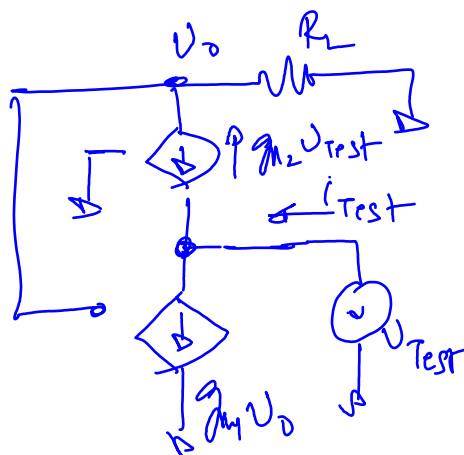b) : Find  $i_{in}$  if  $v_{in} = V_p \sin(\omega_0 t)$ ,  $R_L = 10k\Omega$  and  $R_s = 1k\Omega$ . Assume  $C_1$  and  $C_2$  are large enough to be treated as a short circuit at  $\omega_0$ . [6]



To find  $i_{in}$ , find the  $Z_{in}$

$$g_{m2} v_{test} = v_o / R_L$$

$$\Rightarrow v_o = g_{m2} R_L v_{test}$$

KCL @ i/p. node

$$\begin{aligned} i_{test} &= g_{m2} v_{test} + g_{m1} v_o \\ &= g_{m2} v_{test} + g_{m1} g_{m2} R_L v_{test} \end{aligned}$$

$$\Rightarrow R_{oc} = \frac{1}{g_{m2} + g_{m1} g_{m2} R_L}$$

$$\therefore i_{in} = \frac{v_{in}}{R_s + R_{oc}} = \frac{V_p \sin(\omega t)}{R_s + \frac{1}{g_{m2} + g_{m1} g_{m2} R_L}}$$

There can be multiple ways of approaching this.  
Another possible way is by solving the full-blown  
KVL, KCL.