

# EE210A: Microelectronics I - Mini-Quiz 5

NAME (in capital)

Roll No



Time: 15 minutes

1) : Consider  $\mu_n C_{ox} = 200 \mu A/V^2$ ,  $I_0 = 4mA$ ,  $V_{tn} = 1V$ ,  $V_B = 2.5V$ .

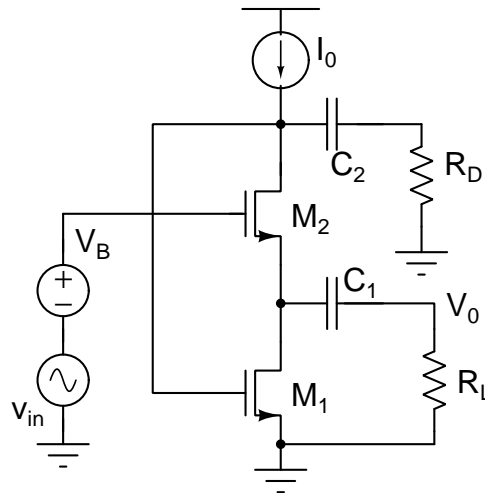


Fig. 1. Problem 1

a) : Size  $M1$  and  $M2$  such that under quiescent conditions  $M1$  is in saturation with a margin of 200 mV, and  $M2$  is in saturation with a margin of 500 mV. [4]

Same as Set A

$$(W/L)_1 = 40$$

$$(W/L)_2 = \frac{40}{0.09}$$

b) : Find  $v_0$  if  $v_{in} = V_p \sin(\omega_0 t)$ ,  $R_L = 1k\Omega$  and  $R_D = 10k\Omega$ . Assume  $C_1$  and  $C_2$  are large enough to be treated as a short circuit at  $\omega_0$ . Find the total currents through  $M1$ ,  $M2$  and  $R_L$  if  $V_p = 10mV$  and  $v_{in}$  is at its maxima. [6]

Expressions same as Set A