

EE210: Analog Electronics - Quiz 7

NAME (in capital)

Roll No

Time: 15 minutes

1) : All transistors in the figures are biased in saturation (biasing network has not been shown). Assume transconductance of M_1 is g_{m1} and that of M_2 is g_{m2} . Neglect CLM.


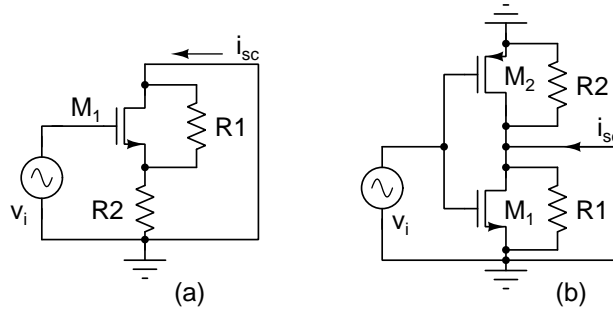


Fig. 1. Problem 1

a) : Find the small-signal short circuit current, i_{sc} , as indicated in Fig. (a).

[5]

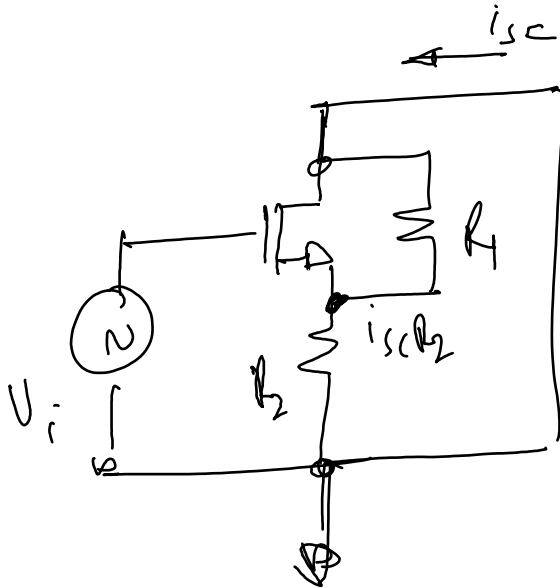

KCL @ the drain

$$i_{sc} = g_m (V_i - i_{sc} R_2) + \left(\frac{0 - i_{sc} R_2}{R_1} \right)$$


$$\Rightarrow i_{sc} \left(1 + \frac{R_2}{R_1} + g_m R_2 \right) = g_m V_i$$

$$\Rightarrow i_{sc} = \left(\frac{g_m V_i}{1 + g_m R_2 + \frac{R_2}{R_1}} \right)$$

contd..

b) : Find the small-signal short circuit current, i_{sc} as indicated in Fig. (b).

[5]

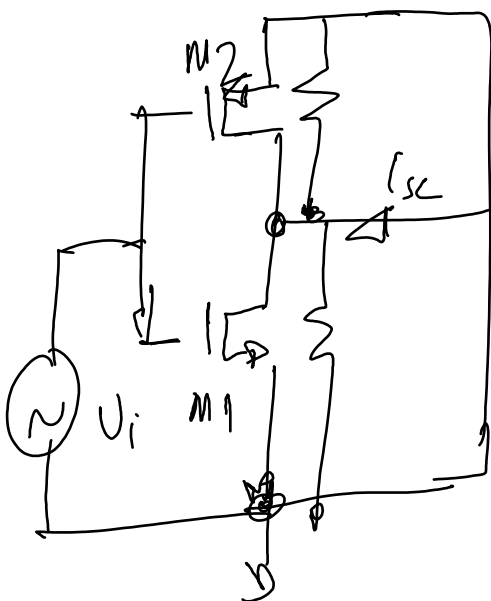

$$\begin{aligned} i_{sc} &= R_1 U_i + R_2 U_i \\ &= (R_1 + R_2) U_i \end{aligned}$$