

EE210A: Microelectronics I - Mini-Quiz 4

NAME (in capital)

Roll No

Time: 20 minutes

1) : For the transistor in the following circuit $\mu_n C_{ox} = 200 \mu A/V^2$, $V_{tn} = 1V$, $W/L = 20$, $I_{DC} = 2mA$. Also, $V_{DD} = 6V$, $V_B = 4V$.


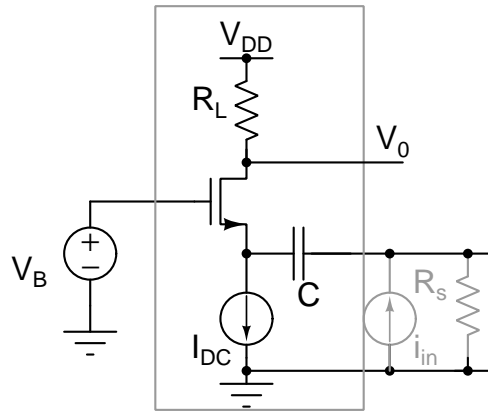


Fig. 1. Problem 1

a) : Find the maximum R_L that you can have to keep the transistor in saturation under quiescent condition. [2]

$$\begin{aligned}
 V_O &= V_{DD} - I_{DC} R_L \geq V_B - V_{tn} \\
 \Rightarrow R_L &\leq \frac{V_{DD} - V_B + V_{tn}}{I_{DC}} \\
 &= \frac{6 - 4 + 1}{2m} = 1.5 K\Omega
 \end{aligned}$$

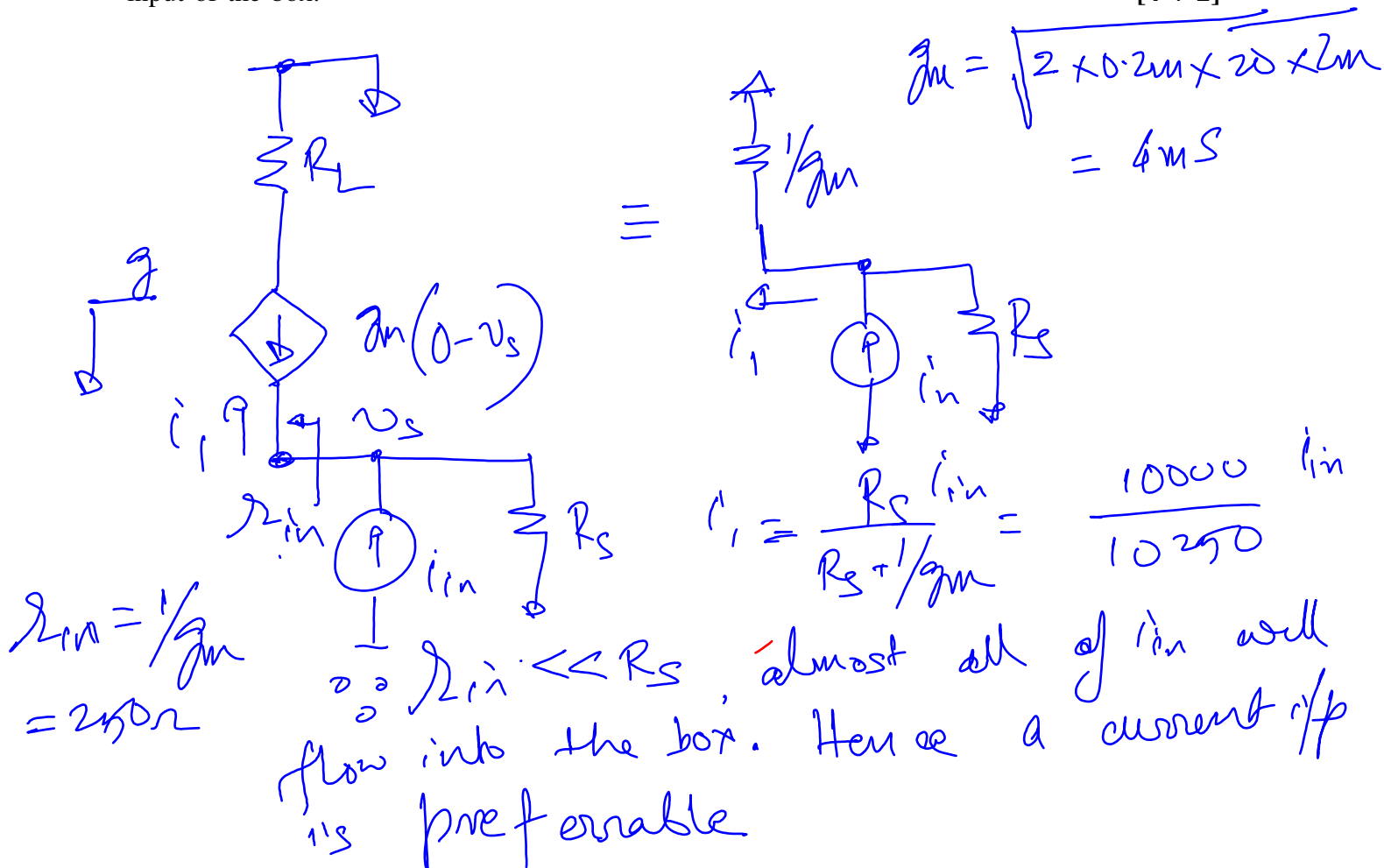b) : Assume $i_{in} = I_p \sin(\omega_0 t)$, $R_s = 10k\Omega$ and C acts as a short circuit at ω_0 . What fraction of the i_{in} flows into the transistor? Is the element inside the box more suited to accept a current input or a voltage input? Assume that the current source has an internal resistance of more than $10k\Omega$ (in parallel) and the voltage source has a resistance more than $10k\Omega$ (in series). Elaborate your argument based on the fraction of the applied input that appears at the input of the box. [4 + 2]



c) : If i_{in} is a step input, with what time-constant will the voltage at V_0 settle to its final value? [2]

